
Contents

| | | |
|----------|---|-----------|
| | Foreword | xvi |
| | Preface to the Fifth Edition | xviii |
| | About the Author | xx |
| 1 | What Is High-End Audio? | 1 |
| 2 | Choosing a High-End Audio System | 7 |
| | Introduction | 7 |
| | Choosing the System Best Suited to Your Needs | 9 |
| | Setting Your Budget | 9 |
| | The Complete vs. the Incremental Purchase | 10 |
| | Value vs. Luxury Components | 12 |
| | Allocating Your Budget to Specific Components | 13 |
| | Upgrading a Single Component | 16 |
| | How to Read Magazine Reviews | 17 |
| | System Matching | 20 |
| | Do's and Don'ts of Selecting Components | 22 |
| | Your Relationship with the Retailer | 23 |
| | Used Equipment | 24 |
| | Product Upgrades | 25 |
| | Component Selection Summary | 26 |
| 3 | Becoming a Better Listener | 27 |
| | Audiophile Values | 29 |
| | Pitfalls of Becoming a Critical Listener | 32 |
| | Sonic Descriptions and their Meanings | 32 |
| | Tonal Balance | 35 |
| | Overall Perspective | 36 |
| | The Treble | 37 |
| | The Midrange | 38 |
| | The Bass | 40 |
| | Soundstaging | 42 |
| | Dynamics | 45 |
| | Detail | 47 |
| | Pace, Rhythm, and Timing | 47 |
| | Coherence | 48 |

| | | |
|----------|--|-----------|
| | Musicality | 48 |
| | Notes on Learning Descriptive Terms | 51 |
| | Critical-Listening Setup Procedures | 52 |
| | Single-Presentation Listening—What It’s All About | 54 |
| | Critical Listening Summary | 55 |
| | Addendum: Level Matching | 56 |
| 4 | Preamplifiers | 57 |
| | Introduction | 57 |
| | How to Choose a Preamplifier | 61 |
| | Balanced and Unbalanced Connections | 62 |
| | What to Listen For | 63 |
| | Tubes vs. Transistors | 65 |
| | Tube Life and Replacement Options | 67 |
| | The Line-Stage Preamplifier | 68 |
| | The Phono-Stage Preamplifier | 69 |
| | RIAA Equalization | 70 |
| | Phono-Stage Gain | 71 |
| | Cartridge Loading | 73 |
| | The Digital Preamplifier | 74 |
| | Audio/Video Controllers and Multichannel Preamplifiers | 75 |
| | How a Preamplifier Works | 75 |
| | Balanced and Unbalanced Preamplifiers | 78 |
| 5 | Power and Integrated Amplifiers | 81 |
| | Introduction | 81 |
| | How to Choose a Power Amplifier | 83 |
| | Integrated Amplifiers | 83 |
| | How Much Power Do You Need? | 85 |
| | The dBW Power Rating | 86 |
| | Why Amplifier Output Current Matters | 87 |
| | What to Look For when Comparing Power Ratings | 89 |
| | Why Amplifier Power Isn’t Everything | 90 |
| | Other Power-Amplifier Considerations | 92 |
| | Tubes vs. Transistors | 92 |
| | Balanced Inputs | 93 |
| | Bridging | 94 |
| | Bi-Amping | 94 |
| | What to Listen For | 96 |
| | A Survey of Amplifier Types | 98 |
| | Single-Ended-Triode Amplifiers | 98 |
| | Single-Ended Solid-State Amplifiers | 101 |
| | Class D (Switching) Power Amplifiers | 101 |
| | Digital Amplifiers | 103 |
| | A Unique Amplifier | 104 |

| | |
|--|------------|
| Output-Stage Topology and Class of Operation | 106 |
| How a Power Amplifier Works | 108 |
| The Power Supply | 109 |
| Input and Driver Stages | 111 |
| Output Stage | 112 |
| How a Tubed Power Amplifier Works | 112 |
| 6 Loudspeakers | 117 |
| Introduction | 117 |
| How to Choose a Loudspeaker | 118 |
| Other Guidelines in Choosing Loudspeakers | 120 |
| Finding the Right Loudspeaker—Before You Buy | 121 |
| What to Listen For | 122 |
| Loudspeaker Types and How They Work | 124 |
| The Dynamic Driver | 124 |
| The Coaxial (Concentric) Driver | 126 |
| Dynamic Compression | 127 |
| Problems with Dynamic Drivers | 128 |
| The Electromagnetic Dynamic Driver | 128 |
| The Planar-Magnetic Transducer | 129 |
| The Heil Air-Motion Transformer | 133 |
| The Electrostatic Driver | 134 |
| The Dipolar Radiation Patterns of Ribbons and Electrostatics | 137 |
| Bipolar and Omnidirectional Loudspeakers | 138 |
| The Horn Driver | 139 |
| Waveguides | 142 |
| The Plasma Driver | 143 |
| The Full-Range Driver | 143 |
| Loudspeaker Enclosures | 144 |
| Infinite-Baffle Loading | 145 |
| Reflex Loading | 145 |
| Passive Radiators | 147 |
| Transmission-Line Loading | 147 |
| Isobarik Loading | 148 |
| The Finite Baffle | 149 |
| System Q | 149 |
| Powered and Servo-Driven Woofers | 150 |
| Enclosure Resonances | 151 |
| Enclosure Shapes | 155 |
| Crossovers | 155 |
| Digital Loudspeakers | 158 |
| DSP Loudspeakers | 160 |
| Subwoofers | 160 |
| Subwoofer Technical Overview | 164 |
| Loudspeaker Stands | 166 |

- 7 Digital Source Components, Part One: Disc Players, DACs, and Interfaces 167**
- Introduction 167
 - How to Choose a Digital Source—Overview 168
 - What to Listen For 169
 - Disc Players 173
 - Super Audio Compact Disc (SACD) 173
 - Universal Disc Players 175
 - Blu-ray Disc 176
 - Bass Management in SACD and Universal Players 176
 - How to Choose a Digital Source—Features and Specs 177
 - Disc Player and DAC Features and Specs 178
 - Digital Interfaces 182
 - The S/PDIF Interface 183
 - The USB Interface 185
 - Ethernet 186
 - The I²S Interface 187
 - DSD over PCM (DoP) 187
 - Proprietary Digital Interfaces 188
 - Wireless Connection 188
 - Jitter in the Digital Interface 189
 - Outboard Clocks 190
 - Asynchronous Sample-Rate Conversion 192
 - High-Resolution Digital Audio: Why 44.1kHz Sampling and 16-bit Quantization Aren't Enough 192
 - 16 Bits, 20 Bits, 24 Bits 195
 - A Caveat About High-Resolution Digital Audio 196
 - Technical Addenda 197
 - Direct Stream Digital (DSD) Encoding on SACD 197
 - High Definition Compatible Digital (HDCD) 199
 - How a DAC Works 201
 - Custom Digital Filters 203
 - Digital-to-Analog Conversion 203
 - Delta-Sigma DACs 204
 - Analog Stages 206
 - Balanced Outputs 206
- 8 Digital Source Components Part Two: Music Servers 209**
- Music Server Sound Quality: Better than Disc 210
 - Downloads 211
 - Download Caveats 211
 - Turnkey Music Servers vs. Computer-Based Servers 212
 - The Turnkey Music Server 212
 - Another Type of Turnkey Music Server 214
-
-

| | | |
|-----------|---|------------|
| | Turnkey Server Considerations | 216 |
| | Using a Smartphone or Tablet with a Music Server | 216 |
| | Internet Radio and Music Subscription Services | 217 |
| | Metadata | 219 |
| | File Formats | 220 |
| | The Do-It-Yourself, PC-Based Music Server | 221 |
| | The Importance of Bit Transparency | 222 |
| | Computer Requirements | 222 |
| | Operating System and Playback Software | 223 |
| | Hard-Disk Storage | 224 |
| | Loading Your Server with Music | 227 |
| | Getting Music from the Server to Your Playback System | 228 |
| | Networking | 229 |
| | A Simple Do-It-Yourself Music Server | 230 |
| | Transferring an LP Collection to a Server | 232 |
| 9 | Turntables, Tonearms, and Cartridges: The LP Playback System | 235 |
| | Introduction | 235 |
| | LP Playback Hardware Overview | 236 |
| | System Hierarchy: Why the LP Front End Is So Important | 237 |
| | How to Choose an LP Playback System | 237 |
| | What to Listen For | 241 |
| | Technical Aspects of Choosing an LP Front End | 243 |
| | The Turntable | 246 |
| | The Base and Plinth | 246 |
| | Sprung and Unsprung Turntables | 247 |
| | The Platter and Bearing Assembly | 249 |
| | Platter Mats, Record Clams, and Vacuum Hold-Down Systems | 250 |
| | The Drive System | 251 |
| | The Tonearm | 252 |
| | The Phono Cartridge | 256 |
| | Moving-Magnet and Moving-Coil Cartridges | 256 |
| | The Strain-Gauge Cartridge | 257 |
| | Stylus Shapes and Cantilever Materials | 258 |
| | LP Playback System Setup | 259 |
| | Record Care and Cleaning | 264 |
| | Vinyl as Art: Half-Speed Mastering, 45rpm Pressings, 180-gram Vinyl, and Direct-to-Disc LPs | 267 |
| 10 | Cables and Interconnects | 271 |
| | Introduction | 271 |
| | How to Choose Cables and Interconnects | 273 |
| | How Much Should You Spend on Cables and Interconnects? | 275 |
| | What to Listen For | 276 |
| | Binding Posts and Cable Terminations | 277 |

| | | |
|-----------|---|------------|
| | Bi-Wired Loudspeaker Cables | 278 |
| | Balanced and Unbalanced Lines | 280 |
| | Cable and Interconnect Construction | 283 |
| | Conductors | 283 |
| | The Dielectric | 284 |
| | Terminations | 284 |
| | Geometry | 285 |
| | Terminated Cables and Interconnects | 286 |
| | Battery Bias in Cables and Interconnects | 287 |
| | Cable and Interconnect Specifications | 289 |
| | Cables in the Power Amplifier/Loudspeaker Interface | 289 |
| 11 | Audio for Home Theater | 291 |
| | Introduction | 291 |
| | Overview of Home-Theater Systems | 292 |
| | Should You Choose a 5.1-, 7.1-, or 9.1-Channel System? | 294 |
| | Home-Theater Controllers | 295 |
| | How to Choose a Controller | 297 |
| | Inputs, Outputs, and Source Switching | 297 |
| | Automatic Calibration | 298 |
| | DSP Speaker and Room Correction | 299 |
| | Analog Bypass Modes | 299 |
| | Bass-Management Flexibility | 300 |
| | 8-Channel Analog Input | 301 |
| | Digital-to-Analog Conversion | 301 |
| | 7.1-Channel and 9.1-Channel Playback from 5.1-Channel Sources | 301 |
| | THX Certification | 302 |
| | 3D Capability, Network Connection, Wireless Streaming, and Multi-Zone | 302 |
| | Multichannel Power Amplifiers | 303 |
| | How to Choose a Home-Theater Power Amplifier | 303 |
| | Loudspeakers for Home Theater | 304 |
| | The Center-Channel Speaker | 304 |
| | Adding a Center Speaker to Your System | 305 |
| | Left and Right Speakers | 306 |
| | Surround Speakers | 306 |
| | Dipolar and Bipolar Surround Speakers | 307 |
| | Surround-Back Speakers | 308 |
| | Height Speakers | 308 |
| | Subwoofers | 308 |
| | Setting Up a Home Theater | 308 |
| | Basic Setup | 309 |
| | Acoustical Treatment | 309 |
| | Speaker Placement | 310 |
| | Surround Speaker Placement | 310 |
| | Center Speaker Placement | 310 |

| | | |
|-----------|---|------------|
| | Left and Right Speaker Placement | 312 |
| | Calibrating a Home Theater | 313 |
| | Bass Management | 313 |
| | Setting Individual Channel Levels | 313 |
| | Adding Home Theater without Compromising Music Performance | 315 |
| | Addendum: Surround-Sound Formats Explained | 316 |
| 12 | Multichannel Audio | 321 |
| | Introduction | 321 |
| | A Short History of Multichannel Audio | 322 |
| | Do We Want Multichannel Music Playback? | 324 |
| | How to Get Multichannel Audio in Your Home | 328 |
| | Loudspeaker Types and Placement | 330 |
| | Bass Management | 330 |
| | Calibration | 332 |
| | Multichannel Playback from 2-Channel Sources | 333 |
| | Ambisonics | 334 |
| 13 | Personal Audio: Headphones, Desktop, and Mobile Audio | 337 |
| | Introduction | 337 |
| | Headphones | 338 |
| | Earbuds, Earphones, and In-Ear Monitors | 338 |
| | Headphones | 340 |
| | Dynamic, Electrostatic, and Planar-Magnetic Headphones | 344 |
| | Headphone Enhancement Technologies | 345 |
| | Crossfeed Circuits | 346 |
| | Smyth Virtual Surround (SVS) | 346 |
| | Binaural Listening | 348 |
| | Multichannel Headphones | 349 |
| | Headphone Specifications | 349 |
| | Headphone Amplifiers | 351 |
| | Balanced and Unbalanced Drive | 352 |
| | Portable Audio | 353 |
| | Desktop Audio | 355 |
| 14 | System Setup Secrets, Part One: Loudspeaker Placement and Room Acoustics | 359 |
| | Introduction | 359 |
| | Loudspeaker Placement | 360 |
| | Loudspeaker Placement in Asymmetrical Rooms | 367 |
| | Short-Wall vs. Long-Wall Placement | 368 |
| | Dipolar and Bipolar Loudspeaker Placement | 370 |
| | Subwoofer Setup and Placement | 371 |
| | Multichannel Loudspeaker Placement | 374 |
| | Loudspeaker Placement Summary | 375 |
| | Common Room Problems and How to Treat Them | 376 |

| | | |
|-----------|--|------------|
| | Acoustical Dos and Don'ts | 385 |
| | A Short Course in Acoustical Theory | 386 |
| | Listening-Room Resonance Modes | 387 |
| | Optimizing Dimensional Ratios | 389 |
| | Standing Waves | 393 |
| | Reverberation | 394 |
| | Building a Listening Room from Scratch | 397 |
| | Isolating the Listening Room | 398 |
| | The Walldamp Technique | 399 |
| | DSP Room Correction | 400 |
| 15 | System Setup Secrets, Part Two: Expert Tuning Techniques, Accessories, Equipment Racks, and AC Power Conditioners | 403 |
| | Introduction | 403 |
| | Accessories | 404 |
| | How to Choose Accessories | 405 |
| | Analog Accessories | 411 |
| | System Setup Techniques | 414 |
| | Equipment Placement | 414 |
| | Cables and Interconnects | 415 |
| | Tubed Equipment | 418 |
| | LP Playback | 419 |
| | Digital Playback | 419 |
| | Loudspeakers | 419 |
| | AC Power | 421 |
| | General | 421 |
| | Equipment Racks and Isolation Devices | 422 |
| | Equipment Racks | 422 |
| | Vibration-Control Accessories: Spikes, Feet, and Cones | 424 |
| | AC Power Conditioners and AC Cords | 425 |
| | AC Power Cords | 428 |
| | Dedicated AC Lines | 428 |
| | A Final Note | 431 |
| 16 | Specifications and Measurements | 433 |
| | Preamplifiers | 433 |
| | Power Amplifiers | 437 |
| | Loudspeakers | 441 |
| | Digital Components | 448 |
| | Appendix A: Sound and Hearing | 455 |
| | Introduction: What is Sound? | 455 |
| | Period and Frequency | 456 |
| | Wavelength | 457 |
| | Phase | 457 |
| | Absolute Polarity | 459 |

| | |
|--|------------|
| Complex Waves | 460 |
| Comb Filtering | 461 |
| Absorption, Reflection, and Diffusion | 461 |
| Diffraction | 462 |
| The Decibel (dB) | 463 |
| Frequency, Loudness, and Equal Loudness Contours | 466 |
| Weighting Filters | 467 |
| The Dynamic Nature of Music | 468 |
| Localization | 469 |
| Other Psychoacoustic Phenomena | 470 |
| Appendix B: Audio and Electronics Basics | 471 |
| Voltage, Current, Resistance, and Power | 471 |
| Ohm's Law | 472 |
| Series and Parallel Circuits | 474 |
| Alternating Current (AC) | 476 |
| Electromagnetic Induction, Inductance, and Capacitance | 477 |
| Filters | 479 |
| Impedance | 480 |
| Loudspeaker Phase Angle | 482 |
| Capacitor Types | 483 |
| Anatomy of an Audio Product | 483 |
| The Power Supply | 484 |
| Amplifier Circuits | 487 |
| Amplifier Distortion | 491 |
| Vacuum Tube Amplifiers | 492 |
| Operational Amplifiers | 493 |
| Digital Electronics | 494 |
| Appendix C: Digital Audio Basics | 495 |
| Introduction | 495 |
| Binary Number System | 496 |
| Sampling and Quantization | 497 |
| Sampling Rate, Nyquist Theorem, and Aliasing | 498 |
| Quantization | 501 |
| Dither | 503 |
| Digital Audio Storage | 505 |
| Error Correction | 506 |
| Digital-to-Analog Conversion | 506 |
| Jitter Explained | 507 |
| Digital Signal Processing (DSP) | 510 |
| Perceptual Coding | 510 |
| Glossary | 513 |
| Index | 545 |
